
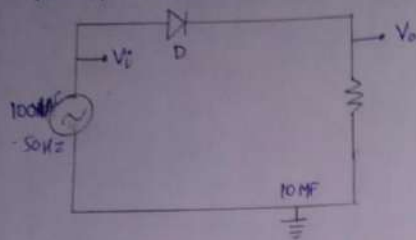


CIRCUIT DIAGRAM

Half-wave rectifier:
WITHOUT FILTER

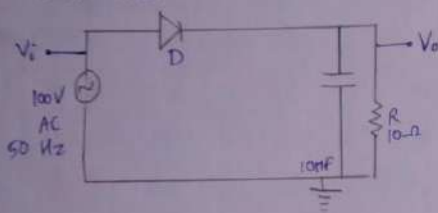


WITH FILTER



TABULATION:

INPUT VOLTAGE		OUTPUT VOLTAGE			
$V_m(t)$	$t(\mu s)$	Without filter $V_m(V)$	$t(\mu s)$	With filter $V_m(V)$	$t(\mu s)$
100V	20MS	100V	100MS	100V, 85V	5MS, 25MS

MODEL GRAPH:

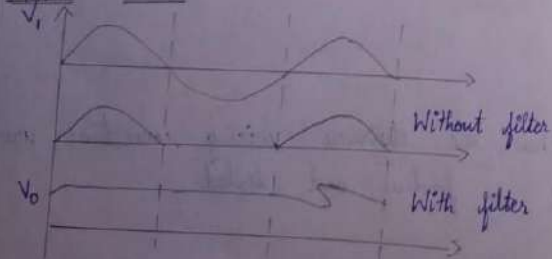

EXPT No. 14

HALF WAVE AND FULL WAVE RECTIFIER

AIM:

- To simulate the following circuits for the purpose of:
- Half wave rectifier
 - Full wave rectifier

APPARATUS REQUIRED:

Laptop with Proteus software

THEORY:

A rectifier is a circuit that converts alternating current (AC) into direct current (DC).

Half-wave rectifier:


Half wave rectifier conducts only during positive half cycle. During positive half cycle the diode conducts and the output voltage is equal to the input voltage. During negative half cycle, the diode does not conduct and the output voltage is equal to zero.

Full-wave rectifier:


Full-wave rectifier conducts during both positive and negative half cycle. During positive half cycle, the output voltage is equal to input voltage. During negative half cycle, the output voltage is equal to negative of the input voltage.

CIRCUIT DIAGRAM:

Full-Wave rectifier WITHOUT FILTER

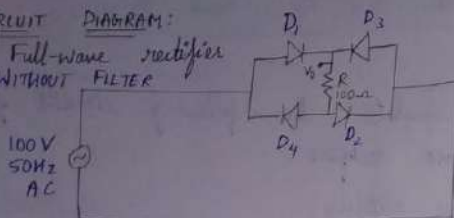


WITH FILTER

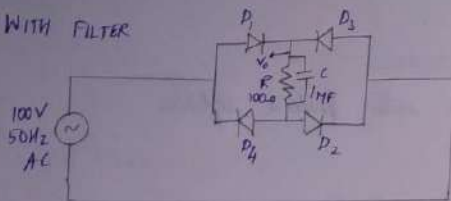

TABULATION:

INPUT VOLTAGE		OUTPUT VOLTAGE			
		Without filter		With filter	
V_m (V)	t (ms)	V_m (V)	t (μs)	V_m (V)	t (μs)
50V	20ms	50V	5ms	100V, 46V	5ms, 14μs

MODEL GRAPH:

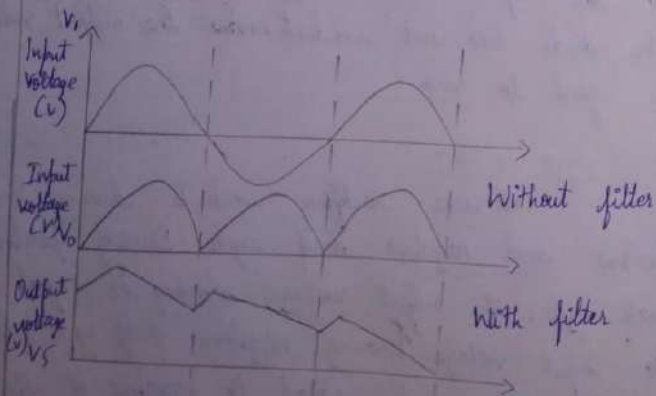

The output of the rectifier circuit is impure DC.

In order to get pure DC the output is filtered by a capacitor filter.

PROCEDURE:


1. Drag the required components from the proteus library.
2. Connect the components as per the circuit diagram.
3. Measure the input and output voltages and note the tabulations.
4. Draw the graph for input and output voltages.

HALF-WAVE RECTIFIER


SCALE

X-axis 2unit 5 μ s


Y-axis 3unit 10V

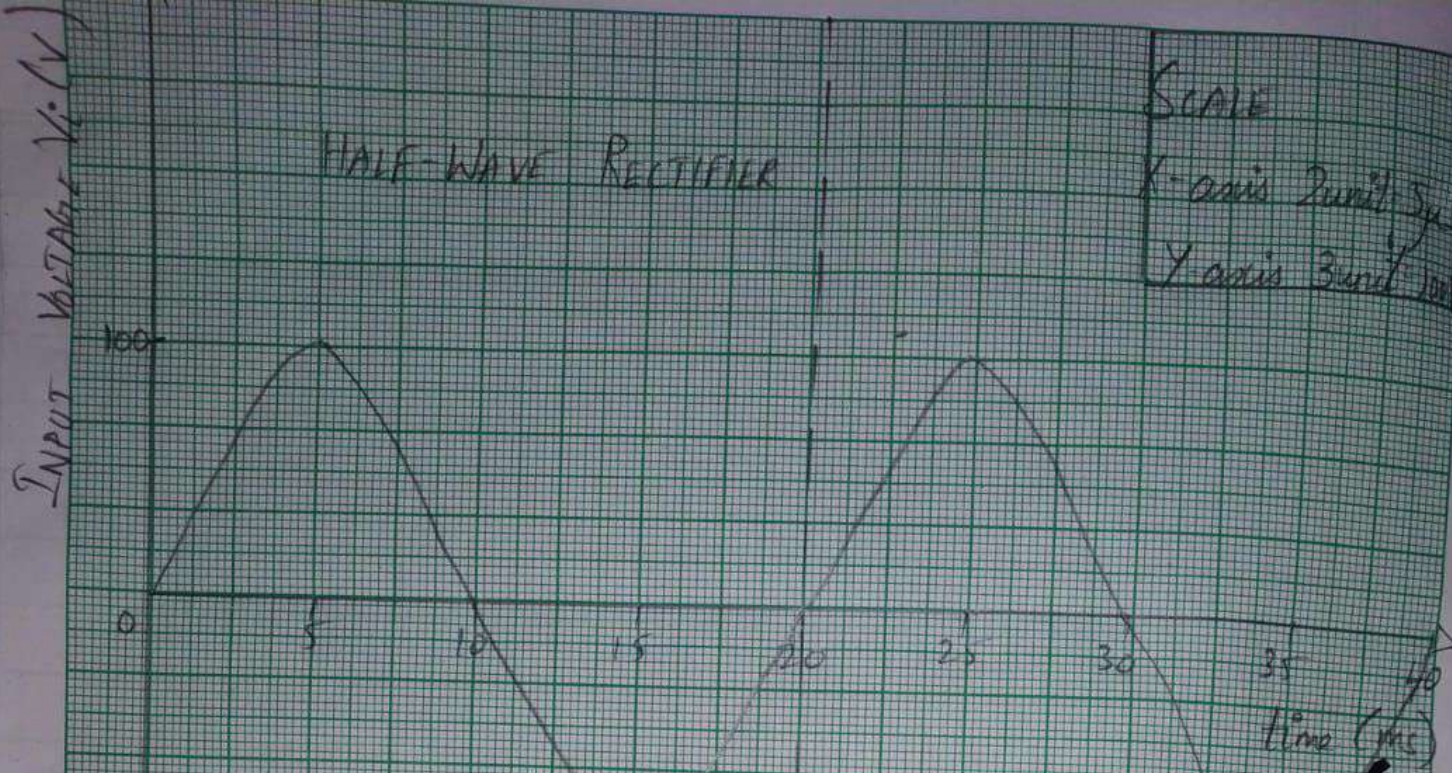

WITHOUT FILTER

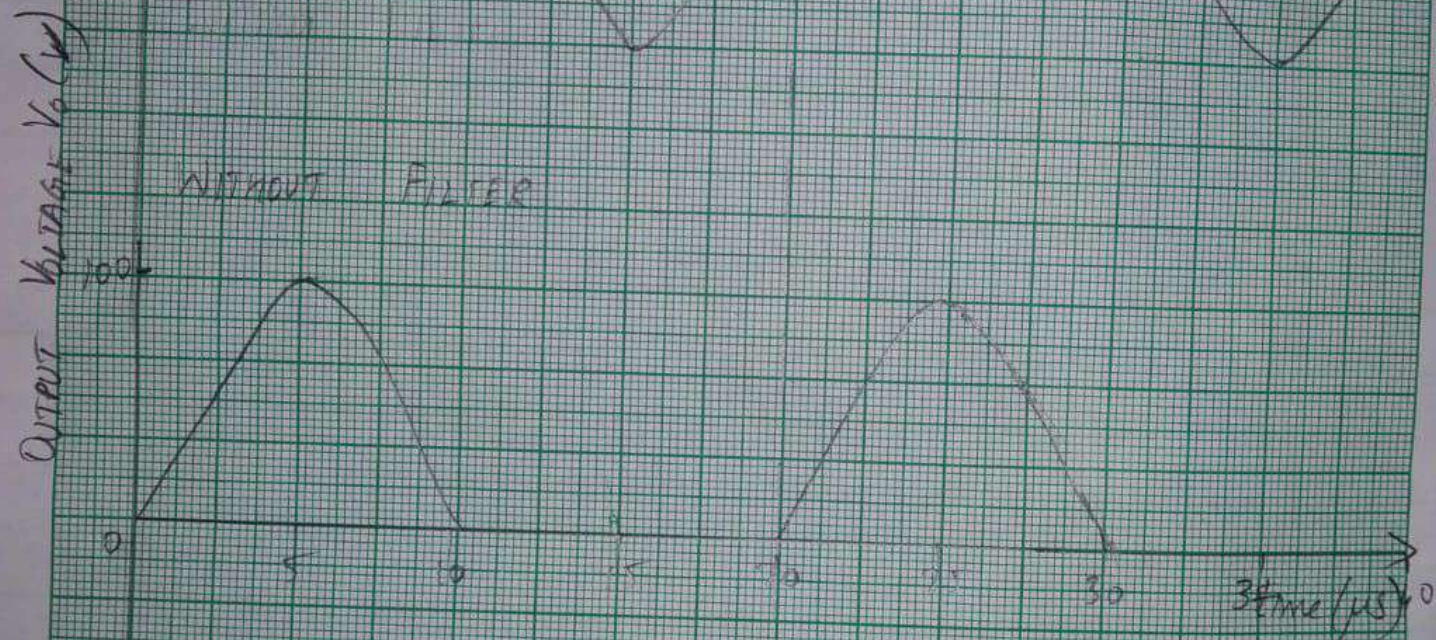

WITH FILTER

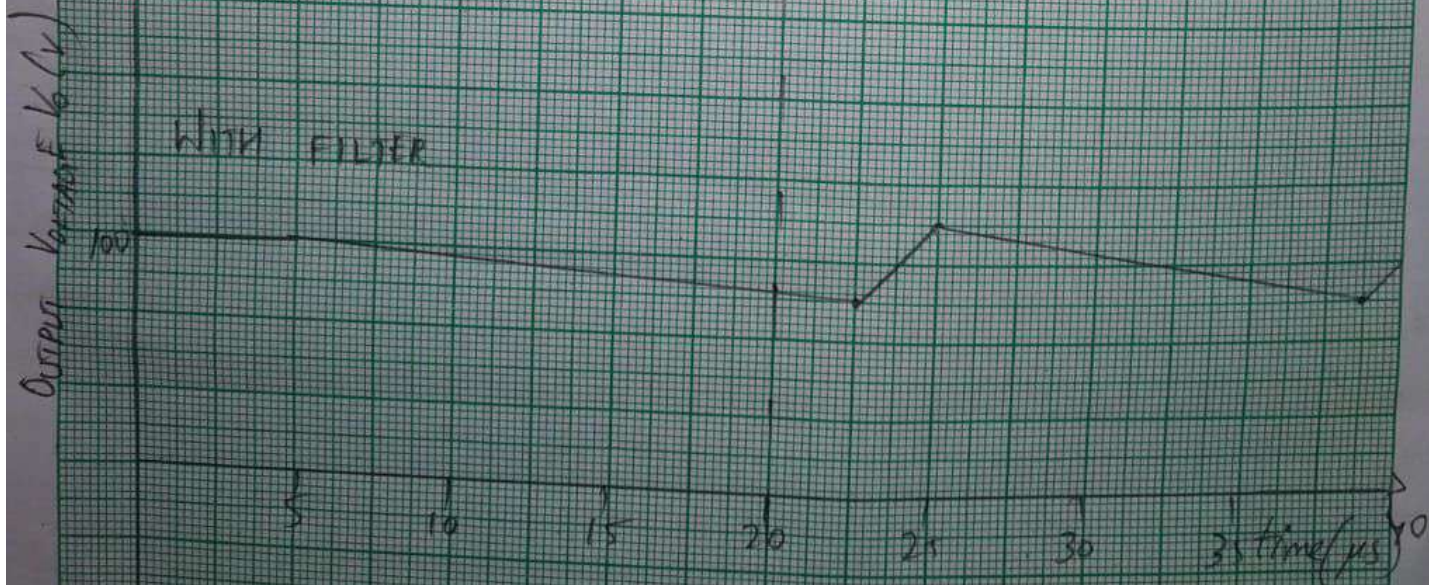


SCALE:

X-axis: 2 unit = 5 μ s

Y-axis: 3 unit = 50V


INPUT VOLTAGE V_i (V)

FULL WAVE RECTIFIER

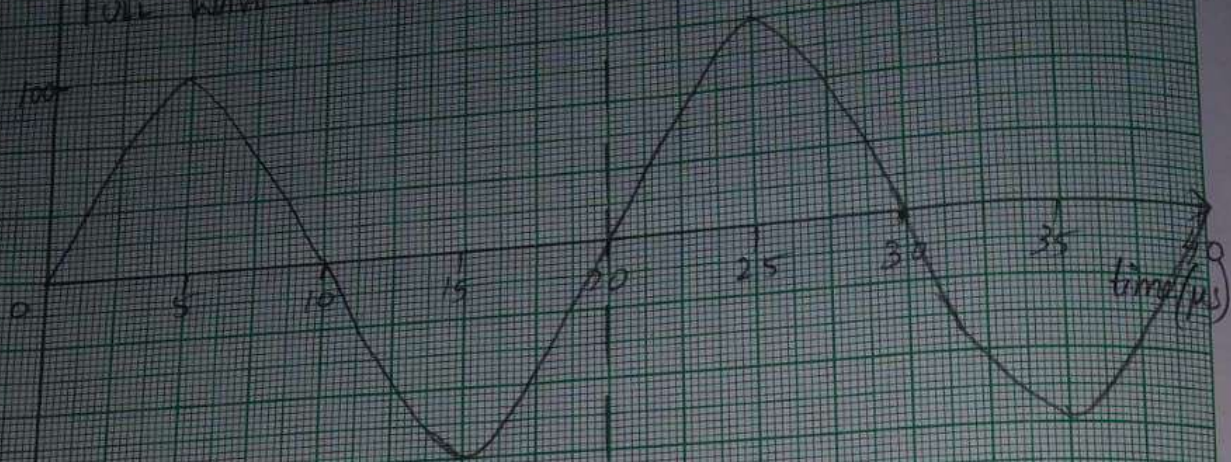

OUTPUT VOLTAGE V_o (V)

WITHOUT FILTER

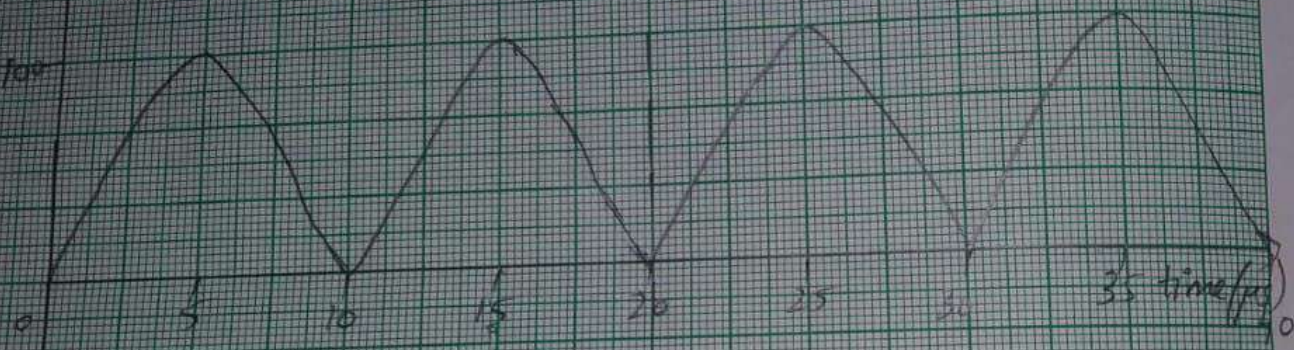

WITH FILTER

